

**MASSACHUSETTS INSTITUTE OF TECHNOLOGY**  
**Department of Physics**

**Problem Solving 8: Driven LRC Circuits**

**OBJECTIVES**

1. To explore the relationship between driven current and driving *emf* in three simple circuits that contain: (1) only resistance; (2) only inductance; and (3) only capacitance.
2. To examine these same relationships in the general case where  $R$ ,  $L$ , and  $C$  are all present, and to do two sample problems on the *LRC* circuits.

**REFERENCE:** Sections 12.1 – 12.4, 8.02 Course Notes.

**General Properties of Driven LRC Circuits**

We have previously considered the “free” oscillations of an *LRC* circuit. These are the oscillations we see if we just “kick” the circuit and stand back and watch it oscillate. If we do this we will see a natural frequency of oscillation that decays in a finite time. Here we consider a very different problem. We now “drive” the *LRC* circuit with a source of *emf* with some (arbitrary) amplitude and frequency. If we drive the circuit with an *emf*  $V(t) = V_0 \sin \omega t$ , where  $\omega$  is any frequency we desire (we get to pick this) and  $V_0$  is any amplitude we desire, then the “driven” response of the system, as opposed to its natural “free” oscillations (which we assume have exponentially decayed to zero) is given by

$$I(t) = I_0 \sin(\omega t - \phi)$$

where


$$I_0 = \frac{V_0}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}, \quad \tan \phi = \left( \frac{\omega L - \frac{1}{\omega C}}{R} \right) \quad (8.1)$$

Note the “driven” response is at the (arbitrary) frequency of the driver, ***and not at any natural frequency of the system.*** However the system will show maximum response to the driving *emf* when the driving frequency ***is*** at the natural frequency of oscillation of the system, i.e. when  $\omega = 1/\sqrt{LC}$ . We can compute the average power consumed by the circuit by calculating the time average of  $I(t)V(t)$  (see Section 12.4, 8.02 Course Notes):

$$\langle P(t) \rangle = \langle I(t)V(t) \rangle = \frac{1}{2} I_0 V_0 \cos \phi \quad (8.2)$$
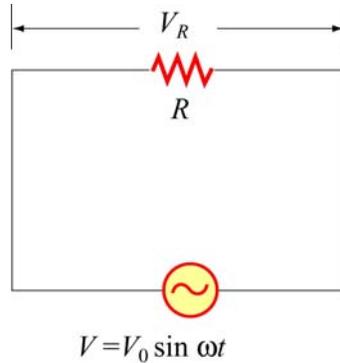
### Example 1: Driven circuit with resistance only

We begin with a circuit which contains only resistance. The circuit diagram is shown below.



The circuit equation is

$$I_R(t)R - V(t) = 0.$$

**Question 1:** What is the amplitude  $I_{R0}$  and phase  $\phi$  of the current  $I_R(t) = I_{R0} \sin(\omega t - \phi)$ ?

**Answer:** (*answer this and subsequent questions on the tear-off sheet at the end!!!*)

**Question 2:** What values of  $L$  and  $C$  do you choose in the general equation (8.1) to reproduce the result you obtained in your answer above?


**Answer:**

**Question 3:** What is the *time-averaged* power  $\langle P_R(t) \rangle = \langle I_R(t)V_R(t) \rangle$  dissipated in this circuit? You will need to know that the time average of  $\sin^2 \omega t$  is  $\langle \sin^2 \omega t \rangle = 1/2$ .

**Answer:**
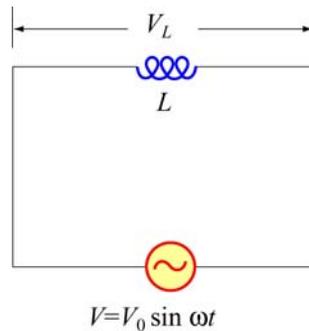
### Example 2: Driven circuit with inductance only

Now suppose the voltage source  $V(t) = V_0 \sin(\omega t)$  is connected in a circuit with only self-inductance. The circuit diagram is



The circuit equation is

$$V(t) = L \frac{dI}{dt}$$

**Question 4:** Solve the above equation for the current as a function of time. If we write this current in the form  $I_L(t) = I_{L0} \sin(\omega t - \phi)$ , what is the amplitude  $I_{L0}$  and phase  $\phi$  of the current? You will need to use the trigonometric identity  $\sin(\omega t - \phi) = \sin \omega t \cos \phi - \sin \phi \cos \omega t$ .

**Answer:**

**Question 5:** What values of  $R$  and  $C$  do you choose in the general equation (8.1) to reproduce the result you obtained in the question above?

**Answer:**


**Question 6:** What is the *time-averaged* power  $\langle P_L(t) \rangle = \langle I_L(t) V_L(t) \rangle$  dissipated in this circuit? You will need to know that the time-average of  $\sin \omega t \cos \omega t$  is  $\langle \sin \omega t \cos \omega t \rangle = 0$ .

**Answer:**

### Example 3: Driven circuit with capacitance only

The ac voltage source  $V(t) = V_0 \sin(\omega t)$  is connected in a circuit with capacitance only.

The circuit diagram is

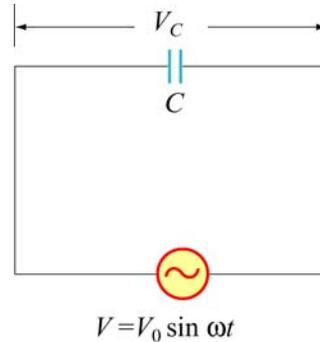

The circuit equation for this circuit is

$$\frac{Q}{C} - V(t) = 0$$

If we take the time derivative of this equation we get

$$\frac{I_C}{C} - \frac{d}{dt} V(t) = \frac{I_C}{C} - \omega V_0 \cos \omega t = 0$$

**Question 7:** Solve the above equation for the current as a function of time. If we write this current in the form  $I_C(t) = I_{C0} \sin(\omega t - \phi)$ , what is the amplitude  $I_{C0}$  and phase  $\phi$  of the current? You will need to use the trigonometric identity  $\sin(\omega t - \phi) = \sin \omega t \cos \phi - \sin \phi \cos \omega t$ .

**Answer:**

**Question 8:** What is the *time-averaged* power  $\langle P_C(t) \rangle = \langle I_C(t) V_C(t) \rangle$  dissipated in this circuit? You will need to know that the time-average of  $\sin \omega t \cos \omega t$  is  $\langle \sin \omega t \cos \omega t \rangle = 0$ .


**Answer:**

### Sample Problem 1

The circuit shown below contains an AC generator which provides a source of sinusoidally varying emf  $\mathcal{E}(t) = \varepsilon_0 \sin \omega t$ , a resistor with resistance  $R$ , and a "black box", which contains *either* an inductor *or* a capacitor, *but not both*. The amplitude of the driving emf,  $\varepsilon_0$ , is 100 Volts/meter, and the angular frequency  $\omega$  is 10 rad/sec. We measure the current in the circuit and find that it is given as a function of time by the expression:  $I(t) = (10 \text{ Amps}) \sin(\omega t - \pi/4)$  [Note:  $\pi/4$  radians =  $45^\circ$ ,  $\tan(\pi/4) = +1$ ].

**Question 9:** Does this current lead or lag the emf  $\mathcal{E}(t) = \varepsilon_0 \sin(\omega t)$

**Answer:**

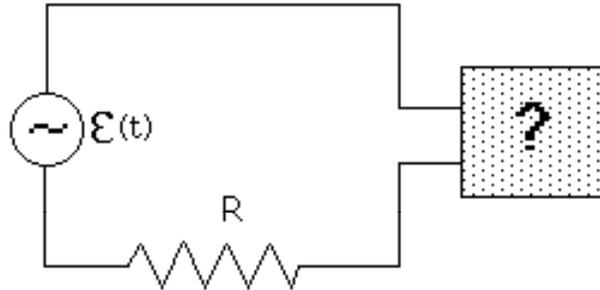

**Question 10:** What is the unknown circuit element in the black box--an inductor or a capacitor?

**Answer:**

**Question 11:** What is the numerical value of the resistance  $R$ ? Your answer can contain square roots, if appropriate. Indicate units.

**Answer:**

**Question 12:** What is the numerical value of the capacitance *or* of the inductance, as the case may be? Your answer can contain square roots, if appropriate. Indicate units.


**Answer:**

## Sample Problem 2

The circuit shown below contains an AC generator which provides a source of sinusoidally varying emf  $\mathcal{E}(t) = \varepsilon_0 \sin(\omega t)$ , a resistor with resistance  $R = 1$  ohm, and a "black box", which contains *either* an inductor *or* a capacitor, *or both*. The amplitude of the driving emf,  $\varepsilon_0$ , is 1 Volt. We measure the current in the circuit at an angular frequency  $\omega = 1$  radians/sec and find that it is exactly in phase with the driving emf. We measure the current in the circuit at an angular frequency  $\omega = 2$  radians/sec and find that it lags the driving emf by exactly  $\pi/4$  radians. [Note:  $\pi/4$  radians =  $45^\circ$ ,  $\tan(\pi/4) = +1$ ].

**Question 13:** What does the black box contain--an inductor or a capacitor, or both? Explain your reasoning.

**Answer:**

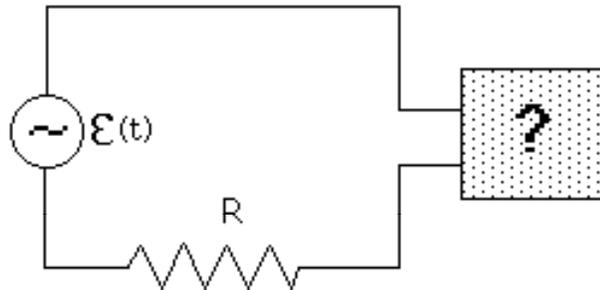

**Question 14:** What is the numerical value of the capacitance *or* of the inductance, *or of both*, as the case may be? Indicate units. Your answer(s) will involve simple fractions only, you will not need a calculator to find the value(s).

**Answer:**

**Question 15:** What is numerical value of the *time-averaged* power dissipated in this circuit when  $\omega = 1$  radians/sec? Indicate units, that is the time-average of  $I(t)V(t)$ . You will need to know that the time-average of  $\sin^2 \omega t$  is  $1/2$ .

**Answer:**

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Physics

Tear off this page and turn it in at the end of class !!!!

**Note:**  
Writing in the name of a student who is not present is a Committee on Discipline offense.

**Problem Solving 8: Driven RLC Circuits**

Group \_\_\_\_\_ (e.g. 6A Please Fill Out)

Names \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

**Example 1: Driven circuit with resistance only**

**Question 1:** What is the amplitude  $I_{R0}$  and phase  $\phi$  of the current  $I_R(t) = I_{R0} \sin(\omega t - \phi)$ ?

**Answer:**  $I_{R0}$ : \_\_\_\_\_  $\phi$ : \_\_\_\_\_

**Question 2:** What values of  $L$  and  $C$  do you choose in the general equation (8.1) to reproduce the result you obtained in your answer above?

**Answer:**  $L$ : \_\_\_\_\_  $C$ : \_\_\_\_\_

**Question 3:** What is the *time-averaged* power  $\langle P_R(t) \rangle = \langle I_R(t)V_R(t) \rangle$  dissipated?

**Answer:**  $\langle P_R(t) \rangle =$  \_\_\_\_\_

**Example 2: Driven circuit with inductance only**

**Question 4:** What is the amplitude  $I_{L0}$  and phase  $\phi$  of the current  $I_L(t) = I_{L0} \sin(\omega t - \phi)$ ?

**Answer:**  $I_{L0}$ : \_\_\_\_\_  $\phi$ : \_\_\_\_\_

**Question 5:** What values of  $R$  and  $C$  do you choose in the general equation (8.1) to reproduce the result you obtained in the question above?

**Answer:**  $R$ : \_\_\_\_\_  $C$ : \_\_\_\_\_

**Question 6:** What is the *time-averaged* power  $\langle P_L(t) \rangle = \langle I_L(t)V_L(t) \rangle$  dissipated?

**Answer:**  $\langle P_L(t) \rangle =$  \_\_\_\_\_

**Example 3: Driven circuit with capacitance only**

**Question 7:** What is the amplitude  $I_{C0}$  and phase  $\phi$  of the current  $I_C(t) = I_{C0} \sin(\omega t - \phi)$ ?

**Answer:**  $I_{C0}$ : \_\_\_\_\_  $\phi$ : \_\_\_\_\_

**Question 8:** What is the *time-averaged* power  $\langle P_C(t) \rangle = \langle I_C(t)V_C(t) \rangle$  dissipated?

**Answer:**  $\langle P_C(t) \rangle =$  \_\_\_\_\_

**Sample Problem 1:**

**Question 9:** Does this current lead or lag the emf  $\mathcal{E}(t) = \mathcal{E}_0 \sin \omega t$

**Answer:** \_\_\_\_\_

**Question 10:** What is the unknown circuit element in the black box--an inductor or a capacitor?

**Answer:** \_\_\_\_\_

**Question 11:** What is the numerical value of the resistance  $R$ ? Your answer can contain square roots, if appropriate. Indicate units.

**Answer:** \_\_\_\_\_

**Question 12:** What is the numerical value of the capacitance *or* of the inductance, as the case may be? Your answer can contain square roots, if appropriate. Indicate units.

**Answer:** \_\_\_\_\_

**Sample Problem 2:**

**Question 13:** What does the black box contain--an inductor or a capacitor, or both? Explain your reasoning.

**Answer:**

**Question 14:** What is the numerical value of the capacitance *or* of the inductance, *or of both*, as the case may be? Indicate units. Your answer(s) will involve simple fractions only, you will not need a calculator to find the value(s).

**Answer:**  $L$ : \_\_\_\_\_  $C$ : \_\_\_\_\_

**Question 15:** What is numerical value of the *time-averaged* power dissipated in this circuit when  $\omega = 1$  radians/sec? Indicate units.

**Answer:** \_\_\_\_\_